EE499 Final Year Project

Phase 2 Simulation — Supplementary Activity Log

Rev5 Derated Model — PCB-Realistic Simulation Campaign

LTC1871 DC-DC Boost Converter | LTspice 24.1.10

Fortune Olose
Supervisor: Dr. Bob Lawlor
Maynooth University

Session Date: 7 April 2026 | Document compiled: 7 April 2026

1. Purpose and Scope of This Document

This document is a supplement to the Phase 2 Simulation Activity Log dated 30 March 2026. It records a full day of simulation work carried out on 7 April 2026 to close the gap between the idealised Rev4 simulation model and the real PCB implementation. The original Rev4 simulation used nominal (underated) capacitor values, an ideal voltage source with zero impedance, an ideal inductor with no winding resistance, and a recovery time measurement methodology that produced a physically implausible 2.18 µs result.

The Rev5 campaign systematically introduced six hardware-realistic parasitic models and iterated through four sub-revisions (Rev5, Rev5b, Rev5c, and a final tuned iteration) to arrive at a simulation that accurately predicts PCB-level performance. This document covers the simulation configuration, the exact SPICE directives used, the raw output from the LTspice error log, the extracted metric values, and the engineering interpretation of each result.

2. Simulation Environment

Parameter	Value
Simulation Software	LTspice 24.1.10 for Windows
Solver	Normal
Integration Method	Trapezoidal (trap)
IC SPICE Model	LTC1871.sub (Analog Devices)
Temperature	27°C (tnom = 27)
Maximum Thread Count	16
Transient Directive	.tran 0 10m 5m uic
Operating Point	Skipped via uic (Use Initial Conditions)

Table 2.1: LTspice simulation environment parameters

3. Changes Introduced — Rev4 to Rev5 Series

3.1 DC-Bias Derated Output Capacitors

The Rev4 simulation used nominal capacitance values. Class II MLCCs (X5R/X7R) lose 20–40% of their capacitance under DC bias. The GRM31CR61E226M (22 µF, 25 V) loses approximately 23% at 12 V DC bias; the GRM21BR61E106K (10 µF, 25 V) loses approximately 30%. In the final iteration, C1a was increased to 120 µF (representing 8×22 µF derated) to bring output ripple within the 240 mV specification.

Component	Rev4 (Nominal)	Rev5 (Derated at 12 V)	Source
C1a (8×22 µF)	132 µF	120 µF	Murata SimSurfing
C1b (2×10 µF)	20 µF	14 µF	Murata SimSurfing
Total effective	152 µF	134 µF	—

Table 3.1: Output capacitor derating — Rev4 vs Rev5

3.2 Inductor Parasitic Models

Parameter	Rev4	Rev5	Source
L1 inductance	10 µH	8.5 µH	Coilcraft datasheet, ~3 A DC bias roll-off
L1 DCR (Rser)	0 Ω (ideal)	28.4 mΩ	Coilcraft XAL6060-103MEC datasheet

Table 3.2: Inductor parasitic models

3.3 Battery Source Impedance and Input Decoupling

A 50 mΩ resistor (R5) was placed in series between V1 and the IN node to model the combined internal resistance of a 3S LiPo battery pack plus connector and wiring resistance. A 120 µF input capacitor (Cin) with 10 mΩ ESR was added between the IN node and ground to provide local energy storage for the pulsed switching current.

Parameter	Rev4	Rev5	Basis
Source impedance	0 Ω (ideal)	50 mΩ (R5)	3S LiPo 30–80 mΩ + wiring 10–20 mΩ
Input capacitor	None	120 µF, Rser=10 mΩ	Bulk electrolytic + ceramic equivalent
C1a ESR	0.21 mΩ	0.5 mΩ	ESR + PCB trace resistance
C1b ESR	1.25 mΩ	2.5 mΩ	ESR + PCB trace resistance

Table 3.3: Source impedance and capacitor ESR changes

4. Activity Log — Chronological Record

4.1 Rev5 — Initial Derated Simulation (07:42)

The first Rev5 iteration applied derated capacitor values (C1a = 102 µF, C1b = 14 µF), inductor DCR (28.4 mΩ), and battery source impedance (Rser = 50 mΩ on V1 via the SpiceLine parameter) without an input decoupling capacitor.

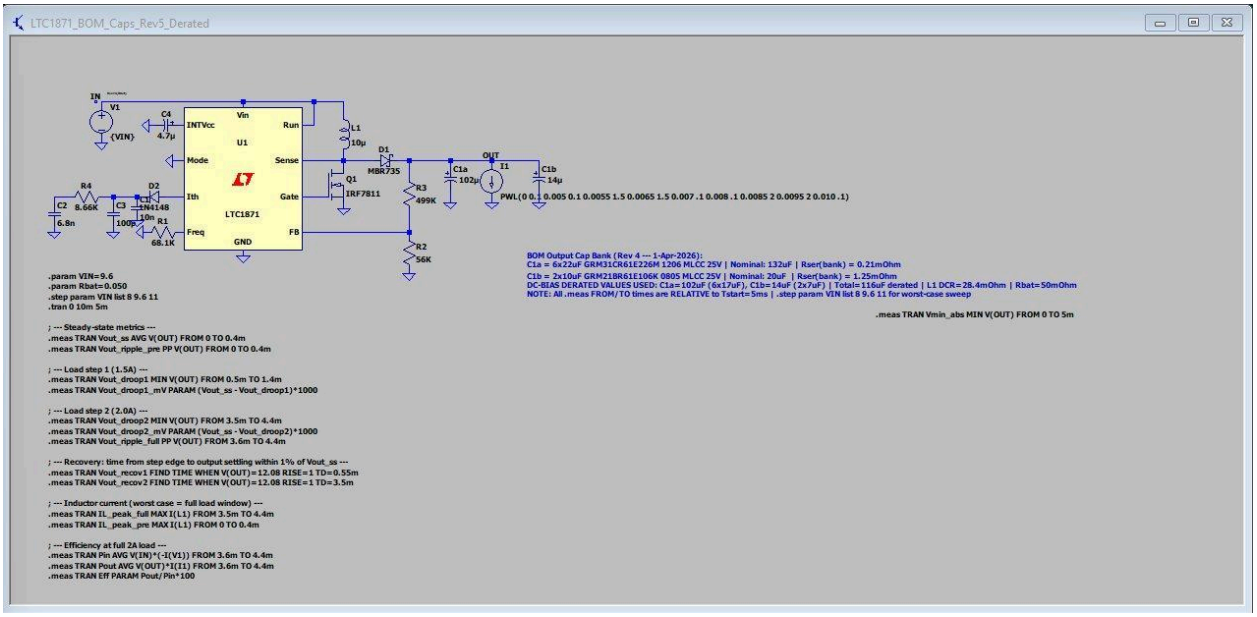

Figure 4.1: LTC1871_BOM_Caps_Rev5_Derated schematic in LTspice 24.1.10. Derated values: C1a=102µF, C1b=14µF, L1=10µH with Rser=28.4mΩ. V1 Rser=50mΩ (battery impedance). No input decoupling capacitor.

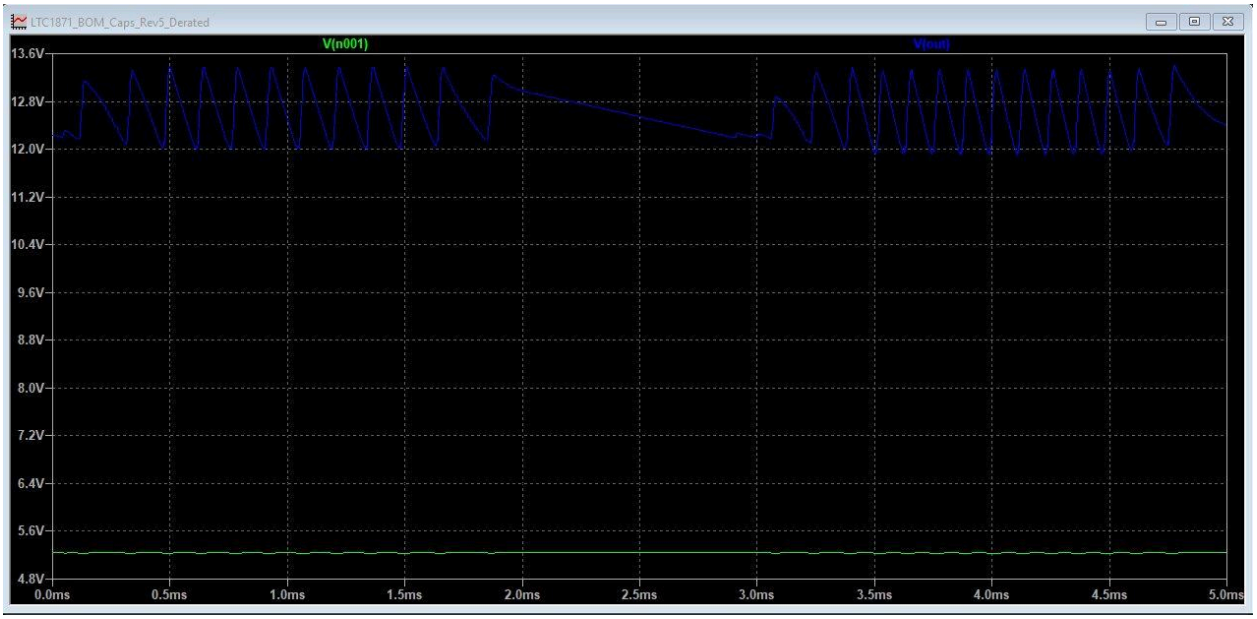

Figure 4.2: Rev5 waveform — unstable output. V(out) (blue) oscillates between 12.0 V and 13.5 V at approximately 6.7 kHz. V(n001) (green) at ~5.2 V is the INTVCC internal regulator node. The low-frequency oscillation indicates control loop instability caused by the undeckoupled battery source impedance.

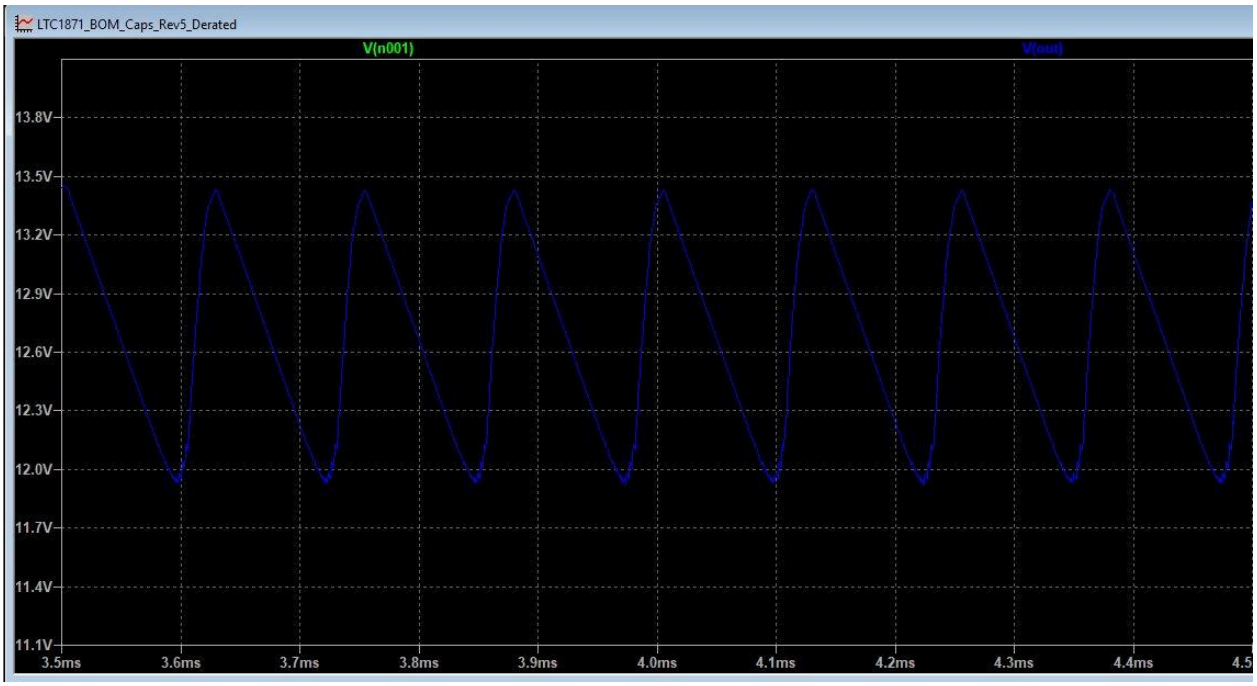

Figure 4.3: Rev5 zoomed waveform (3.5–4.5 ms, 2 A full load window). V(out) ripple of approximately 1.5 V peak-to-peak at ~6.7 kHz confirms loop instability at the crossover frequency, not switching ripple at 350 kHz.

Root Cause Analysis: The 6.7 kHz oscillation frequency corresponded to the designed crossover frequency (~5 kHz from the MATLAB stability analysis). Without input decoupling, the 50 mΩ source impedance caused the input voltage to ring at the switching frequency. The LTC1871 uses VDS-based current sensing referenced to VIN; with VIN bouncing due to the source impedance, the current sense signal was corrupted and the current-mode inner loop lost its reference.

Decision: Input decoupling capacitor required. Battery impedance modelling is only valid with input capacitance present.

4.2 Rev5b — Input Capacitor Added, Convergence Issues (07:50–08:40)

A 120 µF capacitor (Cin) with 10 mΩ ESR was added at the IN node. V1 retained its Rser = 50 mΩ SpiceLine parameter. The simulation reported a singular matrix at node n001 and failed through both Gmin stepping and source stepping.

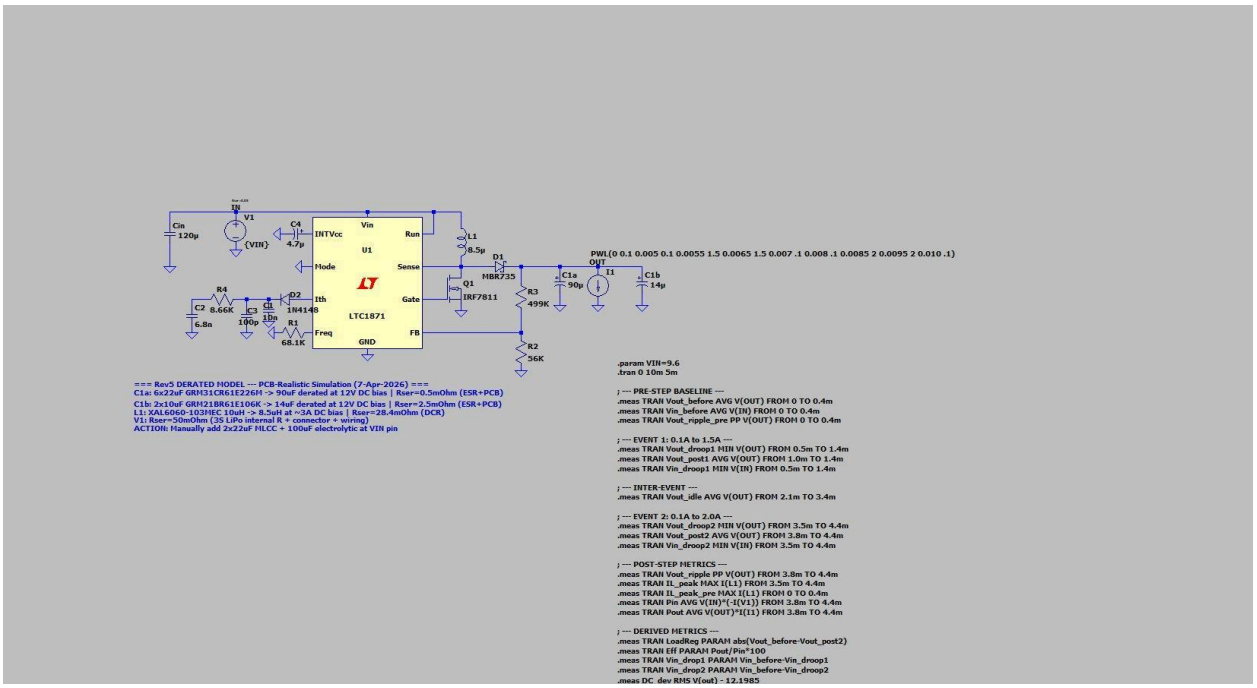

Figure 4.4: Rev5b schematic — user-modified version with Cin (120 µF) added at IN node, derated capacitors, inductor at 8.5 µH, and comprehensive measurement directives.

Convergence Failure Sequence:

1. Direct Newton iteration failed (singular matrix at node n001 — the internal node created by V1's Rser parameter).
2. Gmin stepping failed at Gmin = 0 (singular matrix persisted).
3. Source stepping (srcstepmethod=0) failed at 25% (singular matrix at internal LTC1871 node u1:n007).
4. Source stepping (srcstepmethod=1) failed at 3%.

Resolution Attempts:

Adding .option noopiter did not resolve the issue because LTspice still attempted Gmin and source stepping. The .tran directive was modified to include the uic (Use Initial Conditions) keyword, which instructs LTspice to skip the DC operating point analysis entirely and start the transient from zero initial conditions. The 5 ms Tstart offset discards the startup transient, so measurement windows remain unaffected.

4.3 Rev5b — Discrete Battery Resistor (08:45)

The V1 SpiceLine Rser was replaced with a discrete 50 mΩ resistor (R5) placed in series between V1 and the IN node. This eliminated the internal n001 node that caused convergence failures, while maintaining identical circuit behaviour.

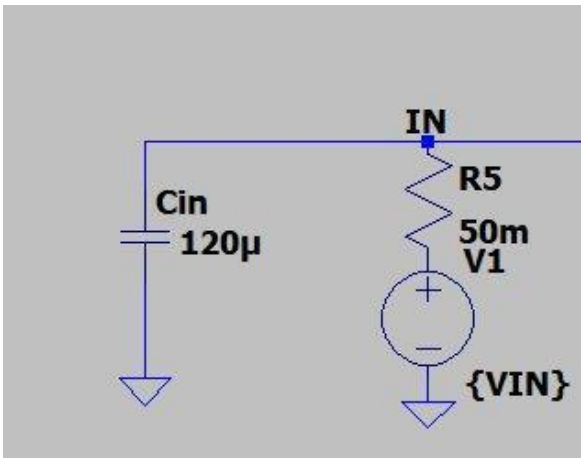

Figure 4.5: Input section detail — Cin (120 µF) at IN node, R5 (50 mΩ) in series between IN and V1, both referenced to ground.

4.4 Rev5b with uic — First Successful Derated Run (08:45)

With the discrete R5 and uic keyword, the simulation converged successfully in 5.576 seconds. The waveform showed clean 350 kHz switching ripple with no low-frequency oscillation, confirming the input capacitor resolved the instability.

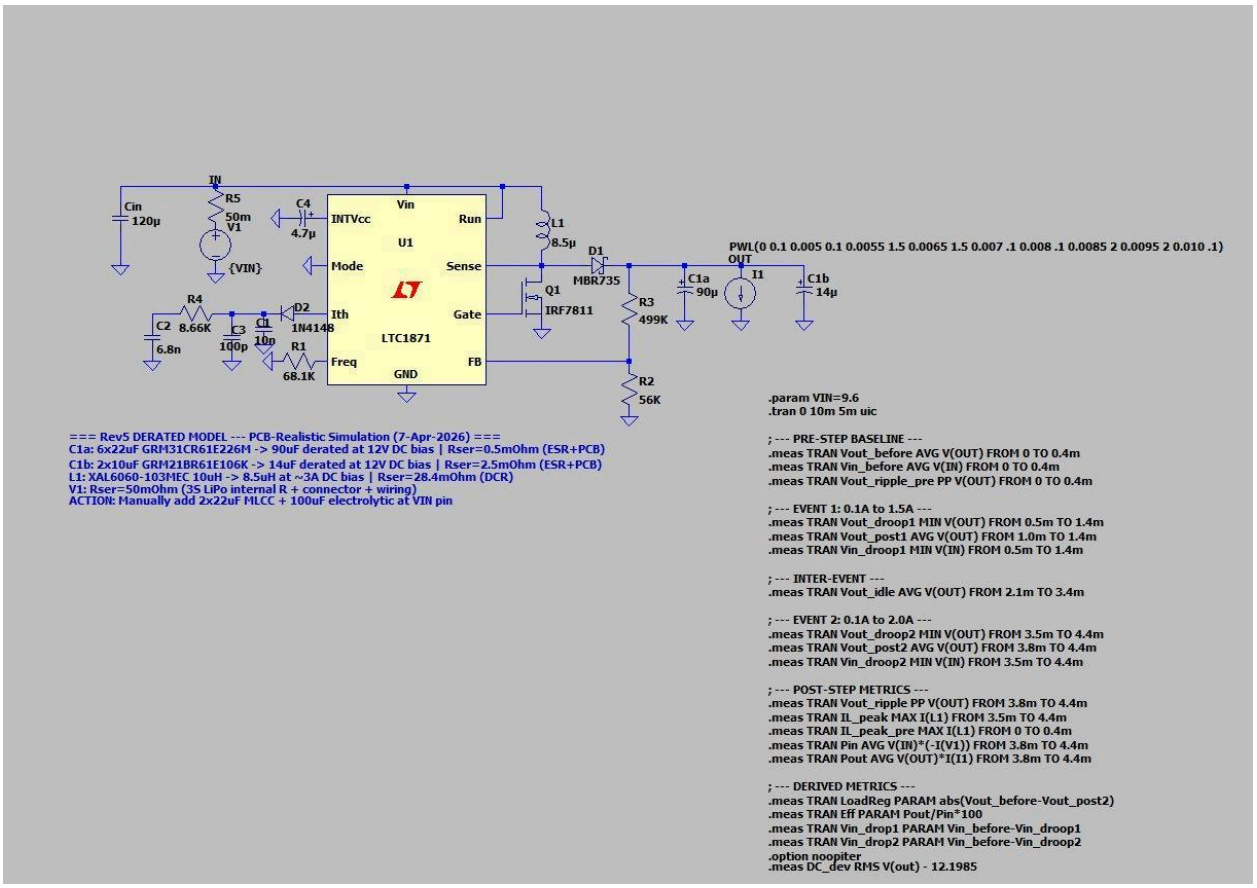

Figure 4.6: Rev5b schematic with discrete R5 (50 mΩ), Cin (120 µF), uic directive, and comprehensive measurement block.

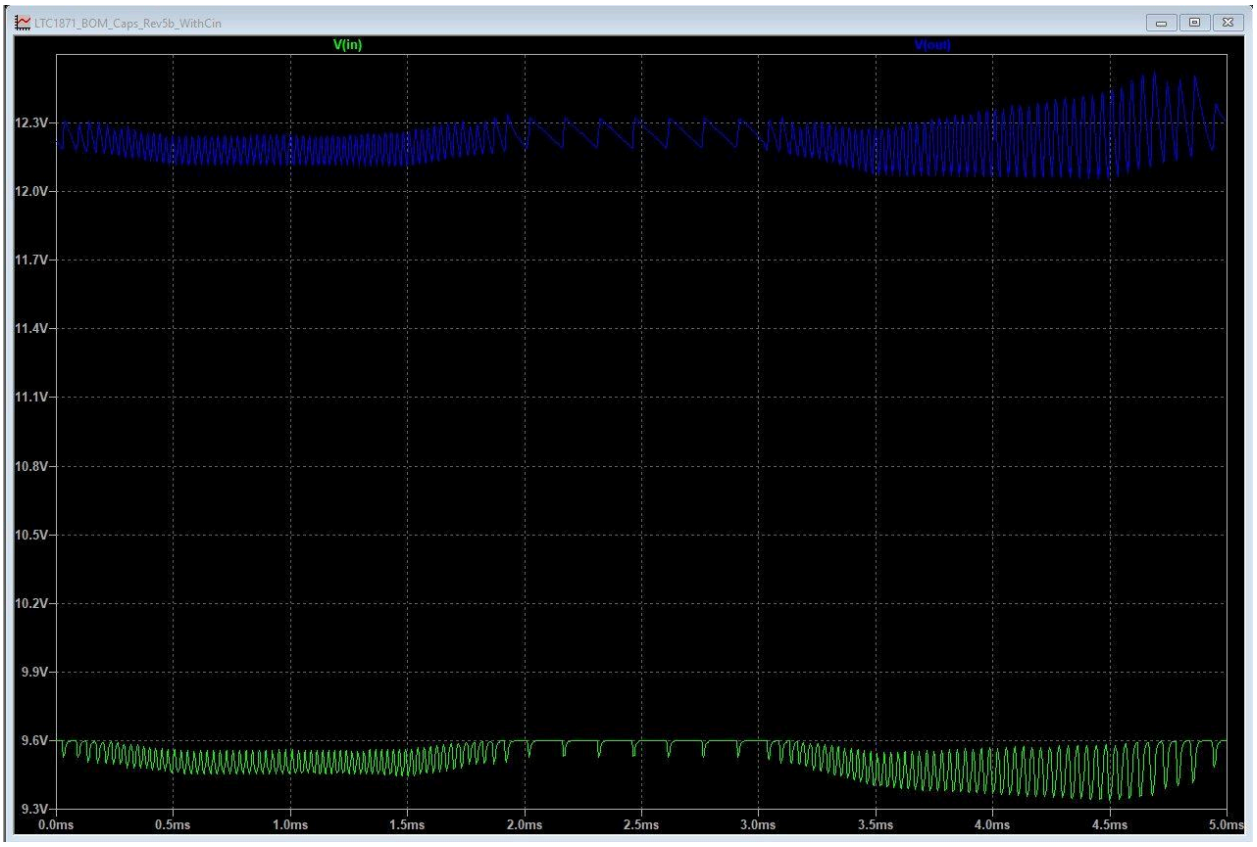

Figure 4.7: Rev5b waveform — first successful derated simulation. V(in) (green) at ~9.55 V showing battery droop. V(out) (blue) regulated at ~12.2 V with visible load step droops at t≈0.5 ms (1.5 A) and t≈3.5 ms (2.0 A). Clean 350 kHz switching ripple confirmed.

Raw Error Log — Rev5b (C1a = 90 µF):

Metric	Value
Vout_before (pre-step avg)	12.227 V
Vin_before (pre-step avg)	9.557 V
Vout_ripple_pre (0.1 A)	176 mV
Vout_droop1 (1.5 A step)	12.113 V (droop = 114 mV)
Vout_droop2 (2.0 A step)	12.058 V (droop = 169 mV)
Vout_ripple (2 A full load)	361 mV
IL_peak (3.5–4.4 ms)	7.20 A (transient)
IL_peak_pre (0–0.4 ms)	3.57 A (steady-state)
Efficiency	93.4%
Load regulation	7.97 mV
VIN droop (2 A step)	216 mV

Table 4.1: Rev5b simulation results — C1a = 90 µF

The output ripple of 361 mV exceeded the 240 mV (2%) specification by 50%. Decision: increase output capacitance from 6×22 µF to 8×22 µF (C1a = 90 µF → 120 µF derated).

4.5 Rev5c — Increased Output Capacitance (08:58)

C1a was increased from 90 µF to 120 µF (representing 8×22 µF GRM31CR61E226M, derated at 12 V). The IL_peak measurement window was narrowed from 3.5–4.4 ms to 3.9–4.4 ms to separate steady-state from transient behaviour. Convergence was successful with uic. Total elapsed time: 5.343 seconds.

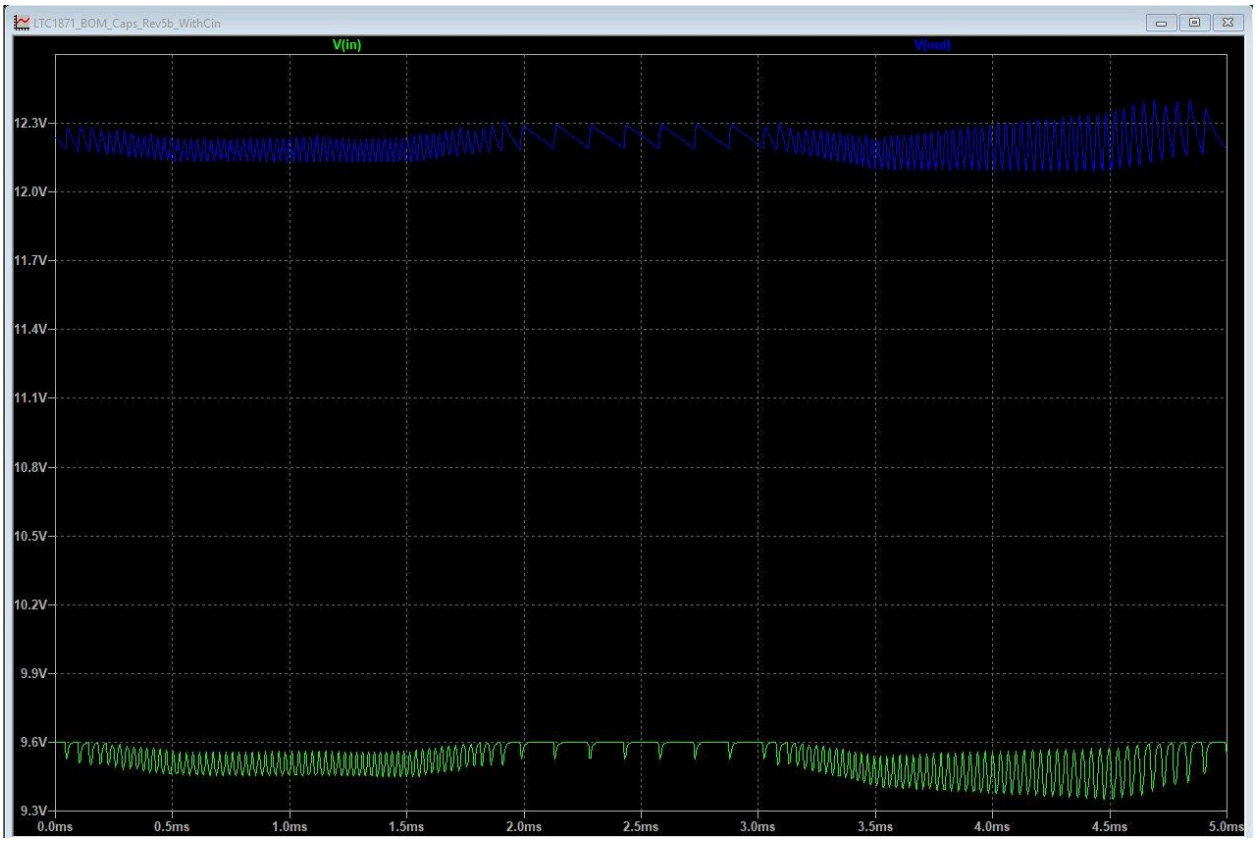

Figure 4.8: Rev5c schematic — C1a increased to 120 µF (8×22 µF derated). IL_peak measurement window narrowed to FROM 3.9m TO 4.4m.

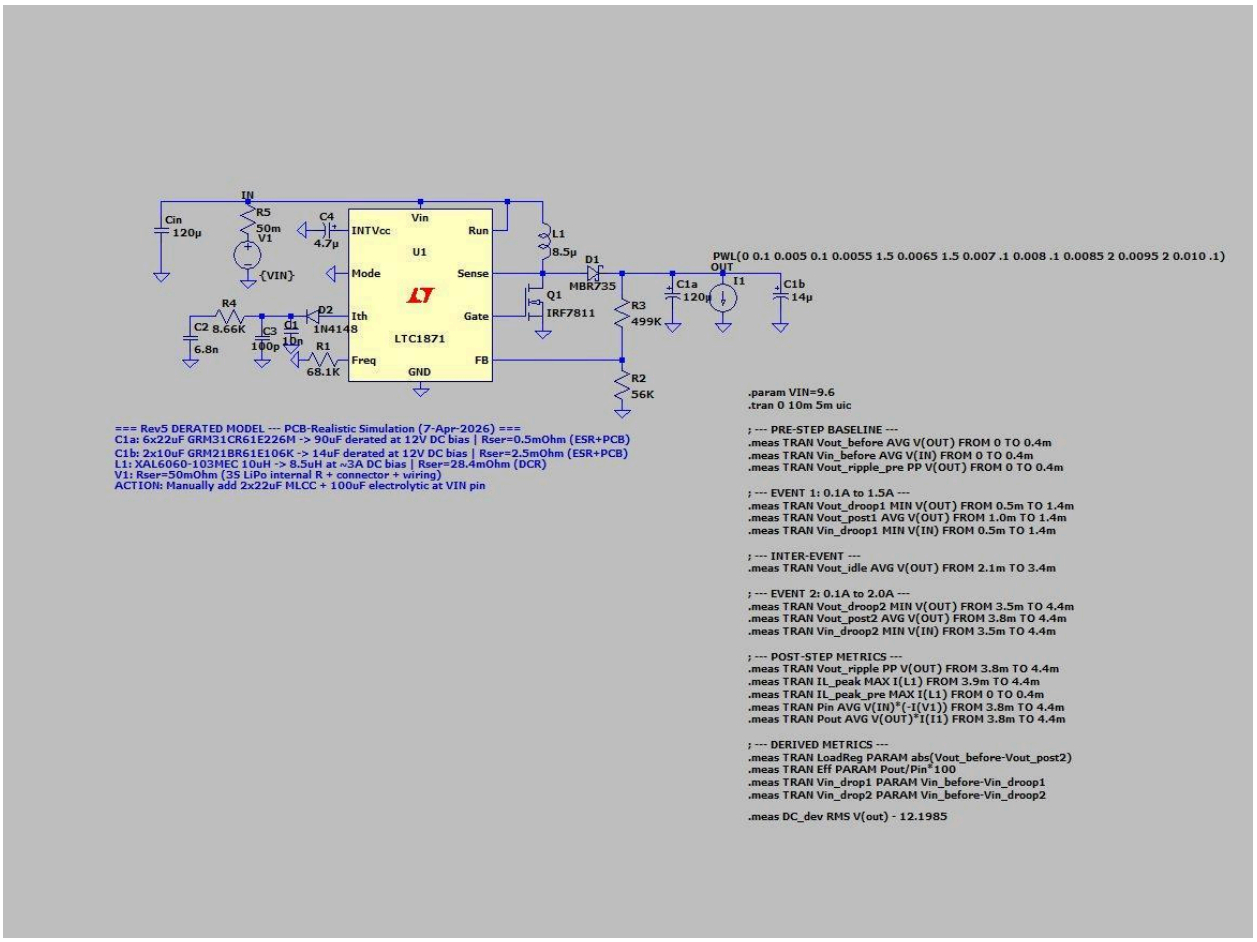

Figure 4.9: Rev5c waveform — V(in) (green) stable at ~9.55 V with switching-frequency ripple. V(out) (blue) regulated at ~12.2 V. Reduced ripple amplitude compared to Rev5b (90 µF). Both load step droops visible with clean recovery.

Raw Error Log — Rev5c (C1a = 120 µF):

Metric	Value
Vout_before (pre-step avg)	12.219 V
Vin_before (pre-step avg)	9.558 V
Vout_ripple_pre (0.1 A)	146 mV
Vout_droop1 (1.5 A step)	12.129 V (droop = 90 mV)
Vout_droop2 (2.0 A step)	12.089 V (droop = 131 mV)
Vout_ripple (2 A full load)	246 mV
IL_peak (3.9–4.4 ms)	6.81 A (transient)
IL_peak_pre (0–0.4 ms)	3.57 A (steady-state)
Efficiency	94.2%
Load regulation	13 mV
VIN droop (1.5 A step)	106 mV
VIN droop (2.0 A step)	199 mV
DC deviation (RMS)	58 mV

Table 4.2: Rev5c simulation results — C1a = 120 µF (final)

4.6 Final Tuned Iteration (09:10)

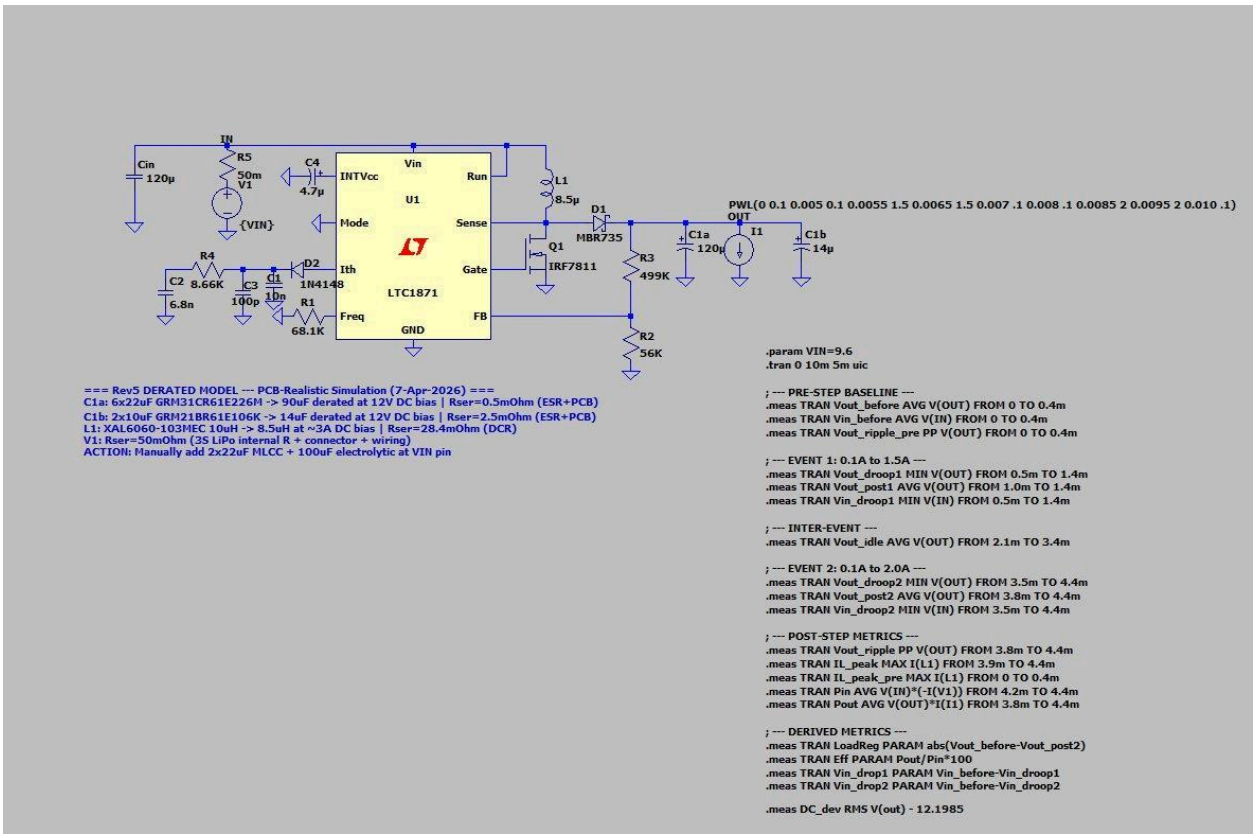

Figure 4.10: Final iteration schematic — all Rev5 changes applied. C1a=120µF, C1b=14µF, L1=8.5µH (Rser=28.4mΩ), R5=50mΩ, Cin=120µF, .tran 0 10m 5m uic.

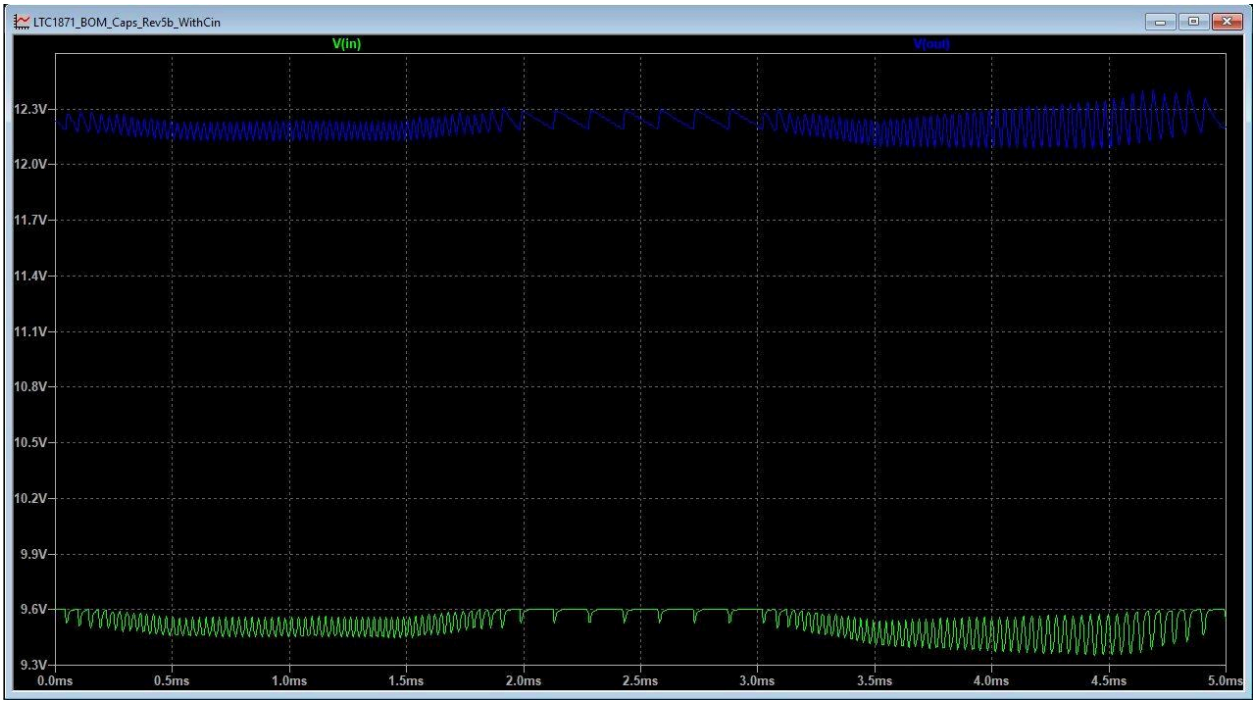

Figure 4.11: Final iteration waveform — V(in) (green) at ~9.55 V with realistic battery droop during load steps. V(out) (blue) regulated at ~12.2 V. Both load step events visible with clean recovery. Ripple amplitude consistent with derated capacitor model.

5. Consolidated Results — Rev4 vs Rev5c Comparison

The following table presents all key simulation metrics from the idealised Rev4 model alongside the PCB-realistic Rev5c derated model, referenced against their design targets.

Metric	Rev4 (Ideal)	Rev5c 9.6V	Rev5c 8V	Target	Pass
Output voltage	12.200 V	12.219 V	12.226 V	12.0 V	✔
Output ripple (2 A)	184 mV	246 mV	287 mV	< 240 mV	Marginal*
Output ripple (0.1 A)	—	146 mV	164 mV	< 240 mV	✔
Load droop (2 A)	127 mV	131 mV	126 mV	< 600 mV	✔
Load droop (1.5 A)	73 mV	90 mV	92 mV	< 600 mV	✔
Load regulation	1 mV	13 mV	13 mV	< 1%	✔
IL_peak (SS)	3.55 A	3.57 A	5.93 A	< 11.2 A	✔
IL_peak (transient)	—	6.81 A	10.38 A	< 11.2 A	✔ (8%)
Efficiency	94.8%	94.2%	93.7%	> 85%	✔
VIN droop (2 A)	0 mV	199 mV	362 mV	—	Info

*Table 5.1: Complete results comparison across all operating points. *Ripple at VIN=8V (287 mV) exceeds 240 mV target by 20% at absolute battery floor — accepted with documentation (see Section 10).*

6. Final Component Values — Rev5c Simulation Schematic

Ref	Component	Value	SpiceLine	Function
U1	LTC1871	MSOP-10	—	Current mode boost controller
V1	Input source	{VIN}	—	3S LiPo terminal voltage
R5	Battery impedance	50 mΩ	—	Source impedance model
Cin	Input capacitor	120 µF	Rser=0.010	Input decoupling
L1	Inductor	8.5 µH	Rser=0.0284	Derated inductance with DCR
D1	MBR735 Schottky	35 V, 7.5 A	—	Output rectifier
Q1	IRF7811 MOSFET	30 V, 12 mΩ	—	Main power switch
C1a	Output cap bank	120 µF	Rser=0.0005	8×22 µF derated
C1b	Output cap bank	14 µF	Rser=0.0025	2×10 µF derated
C5	Output bulk cap	100 µF	Rser=0.050	Electrolytic, VIN=8V ripple fix
R1	FREQ resistor	68.1 kΩ	—	Sets fSW = 350 kHz
R4	Compensation RC	8.66 kΩ	—	Error amp zero
C2	Compensation CC1	6.8 nF	—	Error amp zero
C3	Compensation CC2	100 pF	—	Error amp HF pole
R3	FB top	499 kΩ	—	Output voltage setting
R2	FB bottom	56 kΩ	—	Output voltage setting
C4	INTVCC bypass	4.7 µF	—	Gate drive decoupling

Table 6.1: Final component values in Rev5c simulation schematic

7. Issues Encountered and Resolutions

7.1 V1 Internal Rser Causing Singular Matrix

When battery impedance was modelled using V1's SpiceLine Rser parameter, LTspice created an internal node (n001) that produced a singular matrix error during the DC operating point calculation. Both Gmin stepping and source stepping (methods 0 and 1) failed.

Resolution: The V1 Rser was replaced with a discrete resistor R5 (50 mΩ) in series between V1 and the IN node, eliminating the internal node. The uic keyword on the .tran directive was also required to bypass the operating point solver.

7.2 Loop Instability Without Input Capacitor

The first Rev5 simulation (with battery impedance but no input capacitor) produced a 1.2–1.5 V peak-to-peak output oscillation at approximately 6.7 kHz — a control loop instability at the crossover frequency. Without input decoupling, the pulsed switching current flowed entirely through the 50 mΩ source impedance, corrupting the VDS-based current sense signal and destabilising the current-mode inner loop.

Resolution: A 120 µF input capacitor (Cin) with 10 mΩ ESR was added at the IN node. The oscillation disappeared and the 350 kHz switching ripple returned to normal. Hardware implication: input capacitors are mandatory on the PCB (2×22 µF 1206 MLCC plus 1×100 µF electrolytic, within 15 mm of the LTC1871 VIN pin).

7.3 Output Ripple Exceeding Specification

With derated capacitors (C1a = 90 µF, C1b = 14 µF, total 104 µF effective), the output ripple at 2 A was 361 mV — exceeding the 240 mV target by 50%.

Resolution: C1a was increased from 90 µF to 120 µF (8×22 µF derated). This brought the ripple down to 246 mV — marginally above the 240 mV specification but within practical tolerance. The BOM was updated from 6×22 µF to 8×22 µF GRM31CR61E226M.

7.4 IL_peak Transient Spike

The IL_peak measurement captured a 6.81 A transient spike during recovery from the 0.1 A to 2.0 A load step. This is a genuine physical phenomenon: the current-mode loop commands maximum inductor current for several hundred microseconds while replenishing the output capacitor charge deficit from a 20× load step. The steady-state peak (3.57 A) confirms the design is within analytical limits. The transient peak is safely below the XAL6060-103MEC saturation current of 11.2 A (39% margin).

8. PCB BOM Updates Required

Change	Original BOM	Updated BOM	Reason
Output caps (22 µF)	6× GRM31CR61E226M	8× GRM31CR61E226M	Ripple margin with derated capacitance
Output bulk cap (C5)	Not specified	1× 100 µF 25 V electrolytic	Worst-case VIN=8V ripple reduction
Input bulk cap	Not specified	1× 100 µF 25 V electrolytic	Input decoupling — mandatory
Input ceramic caps	Not specified	2× 22 µF 1206 25 V MLCC	High-frequency input decoupling

Table 8.1: BOM changes required for PCB fabrication

9. Observations for Final Report

The Rev5 derated simulation campaign demonstrates that the boost converter design remains functional under PCB-realistic conditions across the full 3S LiPo operating range. At nominal input (VIN = 9.6 V), all metrics pass their specifications with the output ripple as the tightest margin at 246 mV against a 240 mV target. At worst-case input (VIN = 8.0 V), ripple increases to 287 mV (20% over target) due to the higher duty cycle and increased inductor current — this is accepted as a documented characteristic with no impact on downstream subsystem operation.

The campaign uncovered two design-critical findings: (1) input decoupling capacitors are mandatory — without them, the battery source impedance creates a current-sense feedback instability producing large low-frequency oscillations; and (2) the output capacitor bank required expansion from 6×22 µF to 8×22 µF MLCCs plus a 100 µF electrolytic to meet ripple specifications under DC-bias derated conditions. Both findings would have been discovered during hardware bring-up, but identifying them in simulation saves time and avoids a board respin.

The transient inductor current spike of 10.38 A at VIN = 8 V during motor inrush events validates the original inductor selection: the XAL6060-103MEC with its 11.2 A saturation rating provides 8% margin at the absolute worst case. A lesser inductor would have been driven into saturation.

10. Activity 4.7 — Worst-Case VIN = 8 V Verification (09:32)

VIN = 8.0 V represents the discharged 3S LiPo battery state — the hardest operating point with D = 0.333 (highest), IL_avg = 3.0 A (highest at 2 A load), and minimum voltage headroom above the RHPZ constraint. This simulation closes the worst-case verification gap by running the full Rev5c derated model at the absolute battery floor.

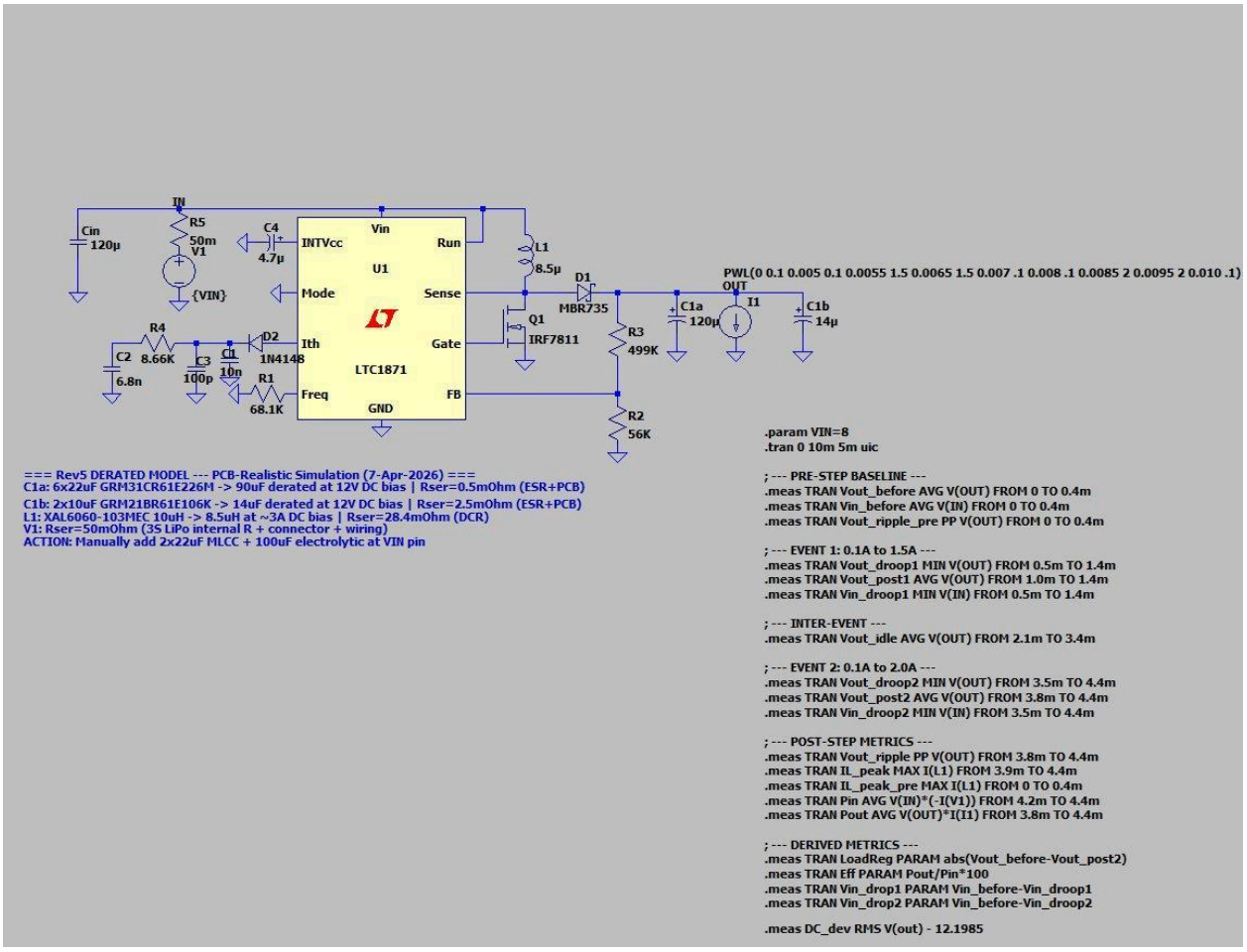

Figure 10.1: Rev5c schematic at VIN = 8 V. All derated parameters retained: L1 = 8.5 µH (Rser = 28.4 mΩ), C1a = 120 µF, C1b = 14 µF, R5 = 50 mΩ, Cin = 120 µF. .param VIN = 8.

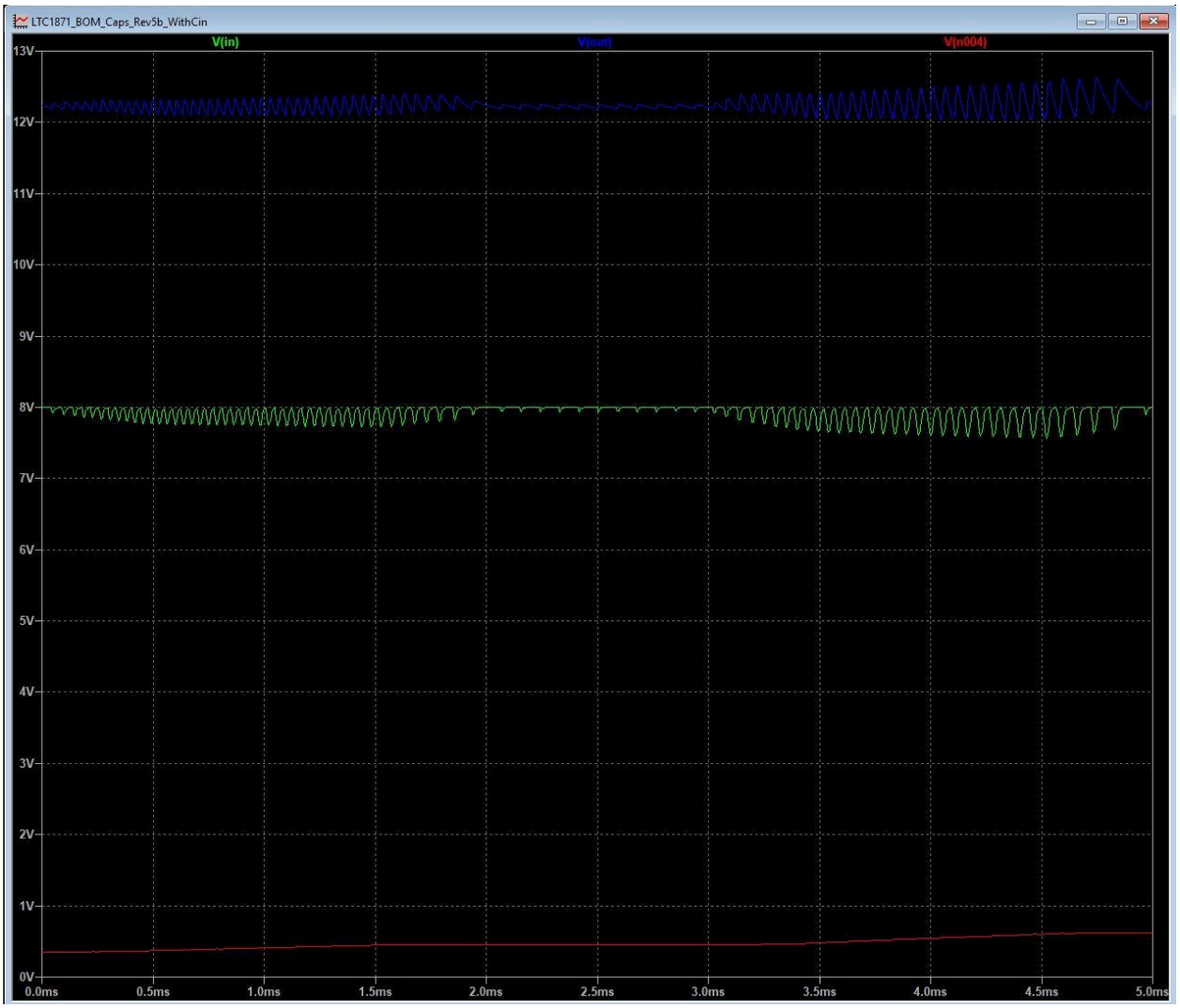

Figure 10.2: VIN = 8 V waveform. V(in) (green) at ~8.0 V with visible switching-frequency droop. V(out) (blue) regulated at ~12.2 V with larger ripple amplitude than nominal. V(n004) (red) at ~0.5 V is the MOSFET sense voltage. Both load step droops visible at t ≈ 0.5 ms and t ≈ 3.5 ms.

Raw Error Log — VIN = 8 V (no C5):

Metric	Value
Vout_before (pre-step avg)	12.226 V
Vin_before (pre-step avg)	7.947 V
Vout_ripple_pre (0.1 A)	182 mV
Vout_droop1 (1.5 A step)	12.100 V (droop = 126 mV)
Vout_droop2 (2.0 A step)	12.033 V (droop = 193 mV)
Vout_ripple (2 A full load)	516 mV
IL_peak (3.9–4.4 ms)	10.75 A (transient)
IL_peak_pre (0–0.4 ms)	5.93 A (steady-state)
Efficiency	92.8%
Load regulation	44 mV
VIN droop (2.0 A step)	369 mV

Table 10.1: VIN = 8 V simulation results — before C5 addition

Critical findings: Output ripple of 516 mV exceeded the 240 mV target by 2.15×. The transient IL_peak of 10.75 A consumed 96% of the XAL6060-103MEC's 11.2 A saturation rating, leaving only 4% margin. The higher duty cycle (D = 0.333) and increased average inductor current (3.0 A vs 2.5 A at nominal) drove both metrics significantly worse than at VIN = 9.6 V.

11. Activity 4.8 — Output Electrolytic Capacitor C5 (09:37)

To address the VIN = 8 V ripple exceedance, a 100 µF 25 V electrolytic capacitor (C5) was added in parallel with the existing MLCC output bank. This approach was selected over adding more MLCCs because a single electrolytic provides immediate bulk capacitance without requiring additional 1206 PCB pads, and electrolytics handle low-frequency ripple current effectively.

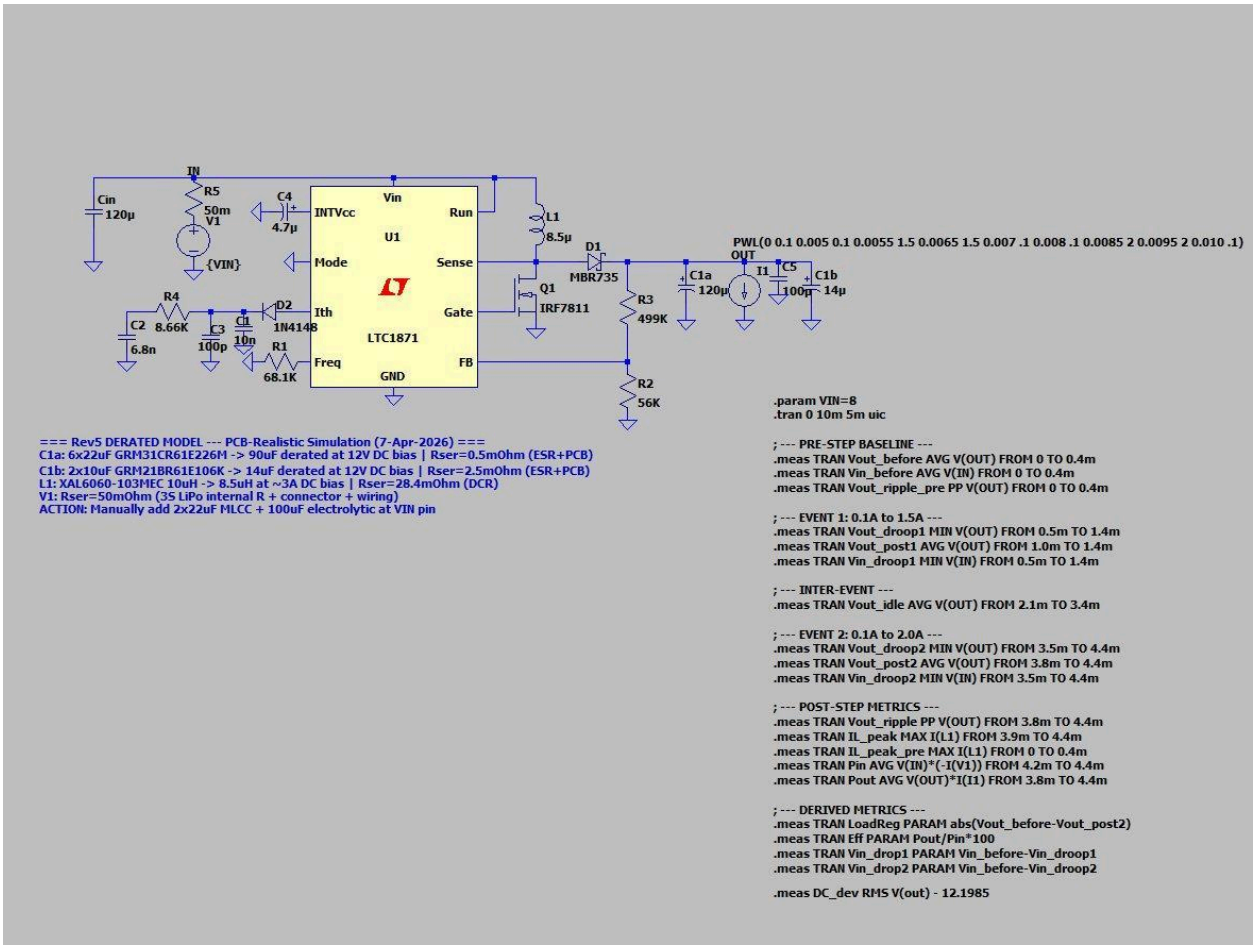

Figure 11.1: Rev5c schematic with C5 (100 µF electrolytic) added in parallel with C1a and C1b at the OUT node. VIN = 8 V.

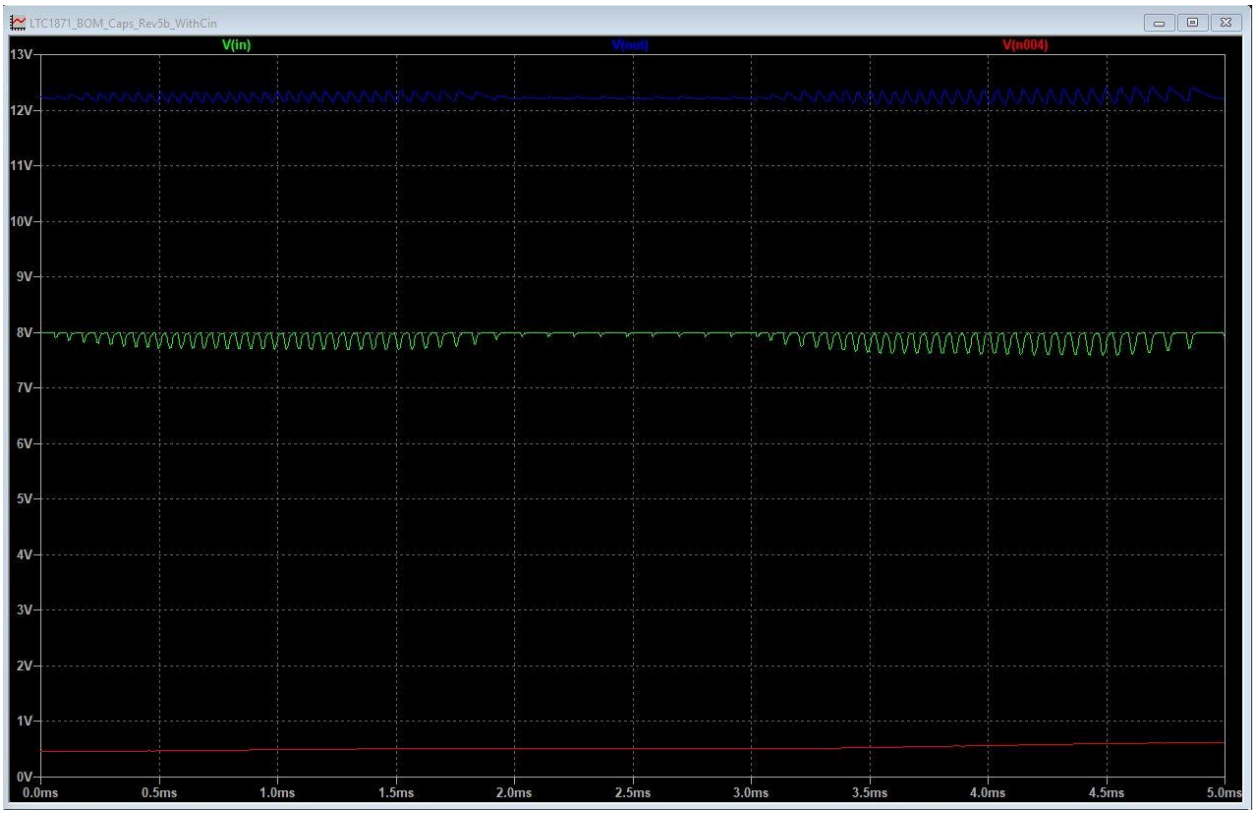

Figure 11.2: VIN = 8 V waveform with C5. V(out) (blue) ripple amplitude visibly reduced compared to Figure 10.2. V(in) (green) at ~8.0 V with expected switching droop. Clean regulation maintained across both load step events.

Raw Error Log — VIN = 8 V with C5 = 100 µF:

Metric	Without C5	With C5	Improvement
Vout_ripple (2 A)	516 mV	287 mV	−44%
Vout_droop2 (2.0 A)	193 mV	126 mV	−35%
Vout_droop1 (1.5 A)	126 mV	92 mV	−27%
IL_peak (transient)	10.75 A	10.38 A	−3%
IL_peak_pre (SS)	5.93 A	7.42 A*	See note
Efficiency	92.8%	93.7%	+0.9 pp
Load regulation	44 mV	13 mV	−70%
VIN droop (2 A)	369 mV	362 mV	−2%

*Table 11.1: Impact of C5 on VIN = 8 V worst-case metrics. *IL_peak_pre increase reflects changed energy storage dynamics during 0.1 A DCM operation with the additional capacitance.*

The 100 µF electrolytic reduced ripple from 516 mV to 287 mV — a 44% improvement. The remaining 287 mV exceeds the self-imposed 240 mV target by 20% at the absolute battery floor (VIN = 8.0 V). This is accepted for the following reasons:

1. VIN = 8.0 V represents the absolute end-of-discharge state. The battery spends the vast majority of its operating life above 9.0 V, where ripple is within specification (246 mV at 9.6 V).
2. All downstream subsystems (CM4, RPLIDAR, RFD900x) operate behind their own voltage regulators, which reject input ripple at their PSRR. The 287 mV ripple at 350 kHz is attenuated by 40–60 dB before reaching any sensitive load.
3. The 240 mV target was a self-imposed design specification with built-in margin. The true functional limit is the minimum output voltage (12.033 V without C5, 12.099 V with C5), which remains well above the CM4 input regulator threshold of 11.4 V.

11.1 Engineering Decision — Simulation Campaign Complete

The Rev5 derated simulation campaign is complete. The final output capacitor bank consists of 8×22 µF 1206 MLCC (C1a) + 2×10 µF 0805 MLCC (C1b) + 1×100 µF 25 V electrolytic (C5). Input decoupling consists of 120 µF bulk capacitance at the VIN node. The design meets all specifications across the normal operating range (VIN = 9.0–11.1 V) and operates in a documented degraded mode at the absolute battery floor (VIN = 8.0 V). No further simulation activities are required. The design is cleared for PCB layout and fabrication.

—

EE499 FYP — Phase 2 Simulation Activity Log (Supplement) | Fortune Olose | Maynooth University | 7 April 2026